

# Multiplier Circuits

Conventional and Approximate Designs

---

# Lecture Outline

---

- Quick Recall
  - Number-representation in computers
  - Arithmetic circuits in computers
    - With the example of Half-adder, Full-adder and Ripple-carry adder
- Conventional Multiplier Circuits
- Approximate Arithmetic Units
  - What are they?
  - Why are they needed?
- Approximate log-based multipliers and its variants

## Quick Recall:

# Number Representation in Computers

---

- Modern computer are **digital circuits** where each nodes can have only **two states**
  - High/Low, or ON/OFF
- The mathematical binary number system is naturally suited for computers

Numbers are represented in binary format

Combination of ones and zeros – called bits

# Quick Recall:

## Number Representation in Computers

---

Numbers are represented in binary format

Combination of ones and zeros – called bits

- Positional number system
  - Position of a bit determines its weight in the value of the number
  - Value of an unsigned N-bit number  $d_{N-1}d_{N-2} \dots d_1d_0$

$$value(A_{us}) = \sum_{i=0}^{N-1} 2^i d_i$$

- Other representation exists: including for signed, fractional numbers
  - Beyond the scope of this lecture
  - Further resources for interested students
    - [https://en.wikipedia.org/wiki/Computer\\_number\\_format](https://en.wikipedia.org/wiki/Computer_number_format)
    - [https://computing-concepts.cs.uri.edu/wiki/Data\\_Representation\\_For\\_Computing](https://computing-concepts.cs.uri.edu/wiki/Data_Representation_For_Computing)
    - [https://en.wikipedia.org/wiki/Signed\\_number\\_representations](https://en.wikipedia.org/wiki/Signed_number_representations)
    - <https://www.stat.berkeley.edu/~nolan/stat133/Spr04/chapters/representations.pdf>

# Quick Recall:

## Arithmetic in Computers

---

- Digital logic circuits
  - Mimic the operations of mathematical binary number system

# Quick Recall:

## Arithmetic in Computers

---

- Digital logic circuits
  - Mimic the operations of mathematical binary number system
- Consider binary addition of two bits
  - 4 possible cases

$$\begin{array}{r} 0 \\ + 0 \\ \hline \end{array}$$

$$\begin{array}{r} 0 \\ + 1 \\ \hline \end{array}$$

$$\begin{array}{r} 1 \\ + 0 \\ \hline \end{array}$$

$$\begin{array}{r} 1 \\ + 1 \\ \hline \end{array}$$

# Quick Recall:

## Arithmetic in Computers

---

- Digital logic circuits
  - Mimic the operations of mathematical binary number system
- Consider binary addition of two bits
  - 4 possible cases

$$\begin{array}{r} 0 \\ + 0 \\ \hline 00 \end{array}$$

$$\begin{array}{r} 0 \\ + 1 \\ \hline 01 \end{array}$$

$$\begin{array}{r} 1 \\ + 0 \\ \hline 01 \end{array}$$

$$\begin{array}{r} 1 \\ + 1 \\ \hline 10 \end{array}$$

# Quick Recall:

## Arithmetic in Computers

---

- Digital logic circuits
  - Mimic the operations of mathematical binary number system
- Consider binary addition of two bits
  - 4 possible cases

$$\begin{array}{r} 0 \\ + 0 \\ \hline 0 \ 0 \\ c \ s \end{array}$$

$$\begin{array}{r} 0 \\ + 1 \\ \hline 0 \ 1 \\ c \ s \end{array}$$

$$\begin{array}{r} 1 \\ + 0 \\ \hline 0 \ 1 \\ c \ s \end{array}$$

$$\begin{array}{r} 1 \\ + 1 \\ \hline 1 \ 0 \\ c \ s \end{array}$$



# Quick Recall:

## Arithmetic in Computers

---

- Digital logic circuits
  - Mimic the operations of mathematical binary number system
- Consider binary addition of two bits
  - 4 possible cases

$$\begin{array}{r} A: 0 \\ + B: 0 \\ \hline 0 \ 0 \\ c \ s \end{array}$$

$$\begin{array}{r} A: 0 \\ + B: 1 \\ \hline 0 \ 1 \\ c \ s \end{array}$$

$$\begin{array}{r} A: 1 \\ + B: 0 \\ \hline 0 \ 1 \\ c \ s \end{array}$$

$$\begin{array}{r} A: 1 \\ + B: 1 \\ \hline 1 \ 0 \\ c \ s \end{array}$$

Truth Table

A	B	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Quick Recall:

## Arithmetic in Computers

- Digital logic circuits
  - Mimic the operations of mathematical binary number system
- Consider binary addition of two bits
  - 4 possible cases

$$\begin{array}{r} A: 0 \\ + B: 0 \\ \hline 0 \ 0 \\ c \ s \end{array}$$


$$\begin{array}{r} A: 0 \\ + B: 1 \\ \hline 0 \ 1 \\ c \ s \end{array}$$

$$\begin{array}{r} A: 1 \\ + B: 0 \\ \hline 0 \ 1 \\ c \ s \end{array}$$

$$\begin{array}{r} A: 1 \\ + B: 1 \\ \hline 1 \ 0 \\ c \ s \end{array}$$

Truth Table

A	B	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

# Quick Recall:

## Arithmetic in Computers

---

- Similarly, consider addition of 3 bits
  - 8 possible cases

Truth Table

Cin	A	B	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


# Quick Recall:

## Arithmetic in Computers

- Similarly, consider addition of 3 bits
  - 8 possible cases

Truth Table

Cin	A	B	carry	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Full-adder

# Quick Recall: Arithmetic in Computers

---


- What about addition of N-bit numbers?

$$\begin{array}{rcccc} & 0 & 0 & 1 & 1 \\ + & 0 & 1 & 1 & 0 \\ \hline \end{array}$$

C    $s_3$     $s_2$     $s_1$     $s_0$



# Quick Recall: Arithmetic in Computers

- What about addition of N-bit numbers?

 

# Quick Recall: Arithmetic in Computers

- What about addition of N-bit numbers?

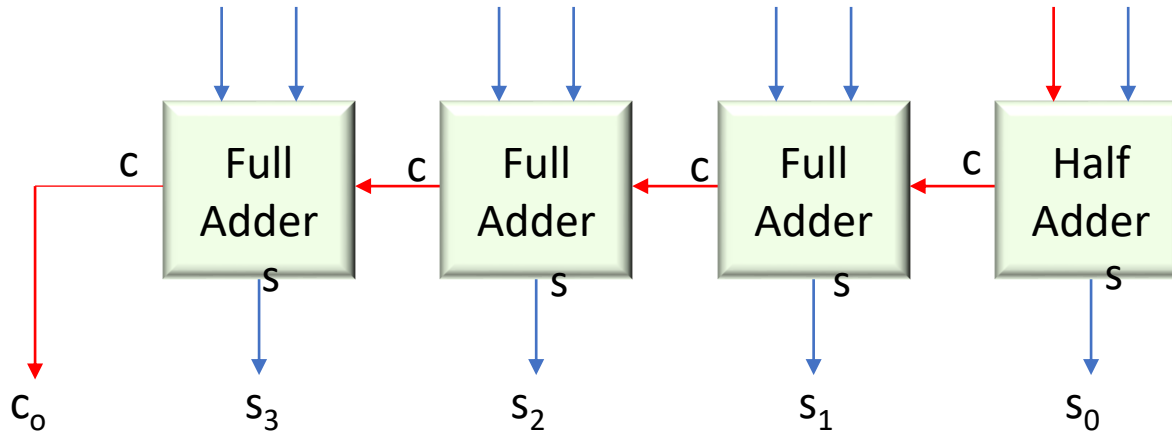 

# Quick Recall:

## Arithmetic circuits

---

- Resource consumption and speed issues
- Logic Area:
  - Number of Gates/logic elements
  - In cases of FPGA, logic elements are CLB – LUTs
    - [https://www.xilinx.com/support/documentation/user\\_guides/ug474\\_7Series\\_CLB.pdf](https://www.xilinx.com/support/documentation/user_guides/ug474_7Series_CLB.pdf)
- Speed:
  - For each logic element, its output appears after a certain delay
  - The speed of the circuit depends on the longest path of logic elements : called as the critical path




# Quick Recall:

## Arithmetic in Computers

---

- Lets analyse the 4-bit RCA circuit

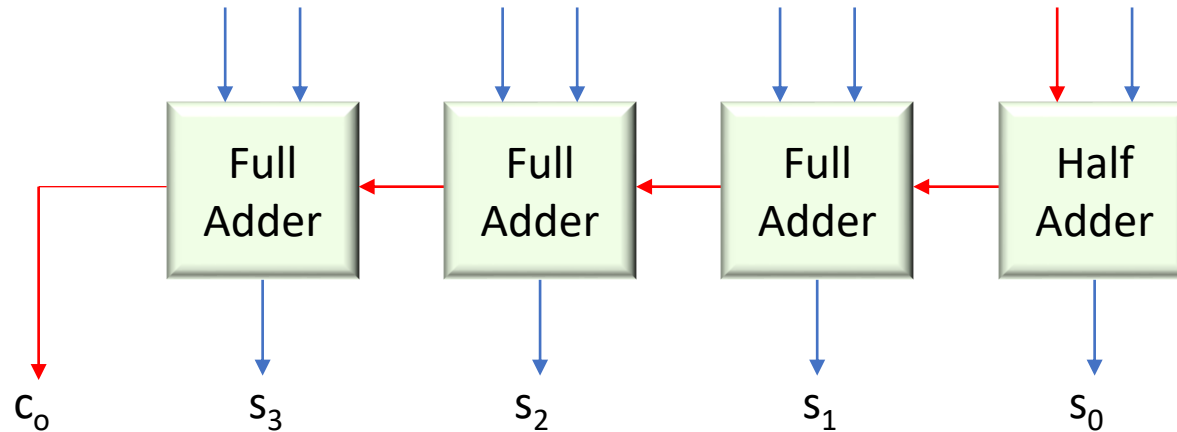

- Logic area:  $(N-1) \text{ FA} + 1 \text{ HA}$
- Delay: delay of  $(N-1) \text{ FA} + \text{delay of HA}$

# Variations in the design

---

- Carry look-ahead adder
  - Improved critical path, more area
  - [https://en.wikipedia.org/wiki/Carry-lookahead\\_adder](https://en.wikipedia.org/wiki/Carry-lookahead_adder)
- Bit-serial adder
  - N cycles
    - RCA and CLA are called parallel adders
  - Smaller area and critical path
  - [https://en.wikipedia.org/wiki/Serial\\_binary\\_adder](https://en.wikipedia.org/wiki/Serial_binary_adder)

# Multipliers

---

# Binary Multiplication


- Consider binary multiplication from high-school

1 0 1 0	→	Multiplicand
× 1 0 1 1	→	Multiplier
-----		
1 0 1 0	→	Partial product 1
1 0 1 0	→	Partial product 2
0 0 0 0	→	Partial product 3
1 0 1 0	→	Partial product 4
-----		
1 1 0 1 1 1 0		
-----		

# Binary Multiplication



- Two steps:
  - Generate partial product
  - Add/Accumulate them

1 0 1 0	→	Multiplicand
× 1 0 1 1	→	Multiplier
-----		
1 0 1 0	→	Partial product 1
1 0 1 0	→	Partial product 2
0 0 0 0	→	Partial product 3
1 0 1 0	→	Partial product 4
-----		
1 1 0 1 1 1 0		
-----		

 
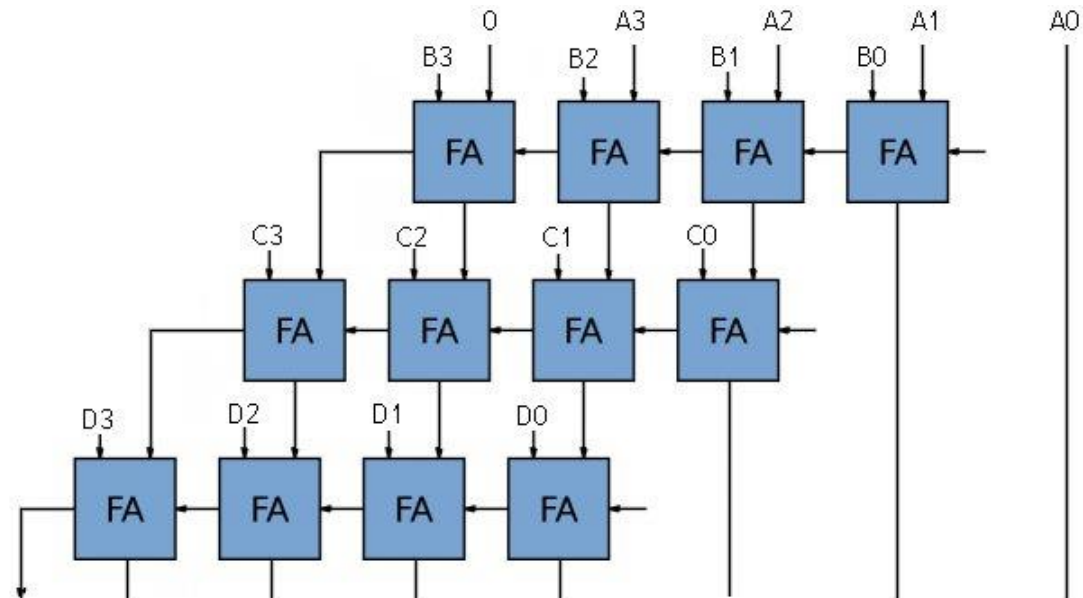 
# Binary multiplier Circuit

- Array multiplier
  - $O(N^2)$  area and delay complexity



# Variations in the designs

---

- Wallace tree reduction
  - [https://en.wikipedia.org/wiki/Wallace\\_tree](https://en.wikipedia.org/wiki/Wallace_tree)
- Dadda tree reduction
  - [https://en.wikipedia.org/wiki/Dadda\\_multiplier](https://en.wikipedia.org/wiki/Dadda_multiplier)

# Good News!!

---

- Modern ASIC/FPGA synthesis tools are smart
  - recognize the + - \* operators in Verilog/VHDL
  - build the circuit behind etc using available logic elements
- Division and Mod are not always supported
  - You may need IP-core
    - [https://en.wikipedia.org/wiki/Semiconductor\\_intellectual\\_property\\_core](https://en.wikipedia.org/wiki/Semiconductor_intellectual_property_core)



# Approximate Arithmetic

---

Use Ripple carry adder for understanding

Then move to approximate multipliers

# Motivation for Approximate Arithmetic


---

- Multiplication/addition dominant operations in many applications
  - For example, Deep neural networks
- Their resource-consumption have direct impact on overall resource-consumption of the system
- How can we improve it?
 
# Motivation for Approximate Arithmetic

---

- RCA/CLA Adder?
- Array multipliers / Wallace / Dadda?
- Essentially all aim to be exact
  - correct for all possible binary input – with no error




# What if we can allow certain errors?

---

# What if we can allow certain errors?

---

- Another dimension in the design space

 

- New possibility of design points
- Gives us further margins for efficiency improvements

# Error resilient applications

---

- You might think errors are not good?

# Error resilient applications

---

- You might think errors are not good?
- Some algorithms are inherently error resilient
- Reasons
  - Algorithm are designed to treat noisy inputs from sensors
  - Treat errors as noise and suppress them
- Minimal impact on output results


# Approximate Adder

---

- Lets understand this concept with a basic RCA adder




# Approximate Adder

 


- Delay: 6 Full-adders

# Approximate Adder

 


- Delay: 6 Full-adders

 


- Errorneous output for some input combinations (Max Error =  $2^3$ )
- Delay: 3 Full-adders → Twice as fast.. always !!
 
# Approximate Arithmetic Units

- Resource-efficient approximate arithmetic units
  - Hardware logic design is modified
    - Simple and efficient design  $\leftrightarrow$  Erroneous output



 - Primary aim when designing approximate arithmetic units
  - Small **error** for more **resource-efficiency**
  - A designs that can offer us the best trade-offs



# Approximate Log-based Multipliers

---

# Approximate Log based Multipliers

---

- Multiplier circuits are more resource-hungry than adders
- Lets recall the log property
  - $\text{Log}(A \times B) = \log(A) + \log(B)$
- So we can use

$$A \times B = \text{antilog}(\log(A) + \log(B))$$

- Reduces to addition 😊
- But, need to compute log and antilog 😞
- Solution: compute log-antilog approximately !!
  - Results in approximate log based multiplier


# Approximate Log based multiplier

- Basic scheme

## Mitchell's Multiplier (MA)
 
### 1. Approximate log of inputs

- Integer part: Position of leading-one ( $k_1, k_2$ )
- Fractional part: Rest of the bits ( $x_1, x_2$ )




# Approximate Log based multiplier

- Basic scheme

## Mitchell's Multiplier (MA)

 
### 1. Approximate log of inputs

- Integer part: Position of leading-one ( $k_1, k_2$ )
- Fractional part: Rest of the bits ( $x_1, x_2$ )



$$k_1 = 11$$
$$x_1 = 0.011$$

$$\log(B_1) = k_1 + x_1$$
$$= 11.011$$

 

$$k_2 = 110$$
$$x_2 = 0.000010$$

$$\log(B_2) = k_2 + x_2$$
$$= 110.000010$$

# Approximate Log based multiplier

- Basic scheme

## Mitchell's Multiplier (MA)

### 1. Approximate log of inputs

- Integer part: **Position of leading-one** ( $k_1, k_2$ )
- Fractional part: Rest of the bits ( $x_1, x_2$ )

### 2. Add

$$\begin{aligned}\log(B_1) &= k_1 + x_1 \\ &= \underline{11}.011\end{aligned}$$

$$\begin{aligned}\log(B_2) &= k_2 + x_2 \\ &= \underline{110}.000010\end{aligned}$$

$$\underline{1001}.0110100$$



# Approximate Log based multiplier

- Basic scheme

## Mitchell's Multiplier (MA)

### 1. Approximate log of inputs

- Integer part: **Position of leading-one** ( $k_1, k_2$ )
- Fractional part: Rest of the bits ( $x_1, x_2$ )

### 2. Add

### 3. Approximate antilog of the sum

- Append 1 to the left of fractional part
- Scale w.r.t the integer part

$$\begin{aligned}\log(B_1) &= k_1 + x_1 \\ &= 11.011\end{aligned}$$

$$\begin{aligned}\log(B_2) &= k_2 + x_2 \\ &= 110.000010\end{aligned}$$

1001 .0110100

1.0110100

101101000 = (720)<sub>10</sub>  
Accurate: 66x11 = (726)<sub>10</sub>

# Approximate Log based multiplier

- Basic scheme

## Mitchell's Multiplier (MA)

### 1. Approximate log of inputs

- Integer part: **Position of leading-one** ( $k_1, k_2$ )
- Fractional part: Rest of the bits ( $x_1, x_2$ )

### 2. Add

### 3. Approximate antilog of the sum

- Append 1 to the left of fractional part
- Scale w.r.t the integer part

### Mathematically

$$\text{approx\_product} = \begin{cases} 2^{k_1+k_2}(1+x_1+x_2), & x_1+x_2 < 1 \\ 2^{k_1+k_2+1}(x_1+x_2), & x_1+x_2 \geq 1 \end{cases}$$

$k_1, k_2$ : **position of leading-one** in  $B_1$  and  $B_2$

$x_1$  and  $x_2$ : fractional part of the log values

# Approximate Log based multiplier

Based on the elementary log-multiplication property:  $\log_b(AB) = \log_b A + \log_b B$

## Mitchell's Multiplier (MA)

### 1. Approximate log of inputs

- Integer part: Position of leading-one ( $k_1, k_2$ )
- Fractional part: Rest of the bits ( $x_1, x_2$ )

### 2. Add

### 3. Approximate antilog of the sum


- Append 1 to the left of fractional part
- Scale w.r.t the integer part

### Mathematically

$$\text{approx\_product} = \begin{cases} 2^{k_1+k_2}(1+x_1+x_2), & x_1+x_2 < 1 \\ 2^{k_1+k_2+1}(x_1+x_2), & x_1+x_2 \geq 1 \end{cases}$$


$k_1, k_2$ : position of leading-one in  $B_1$  and  $B_2$

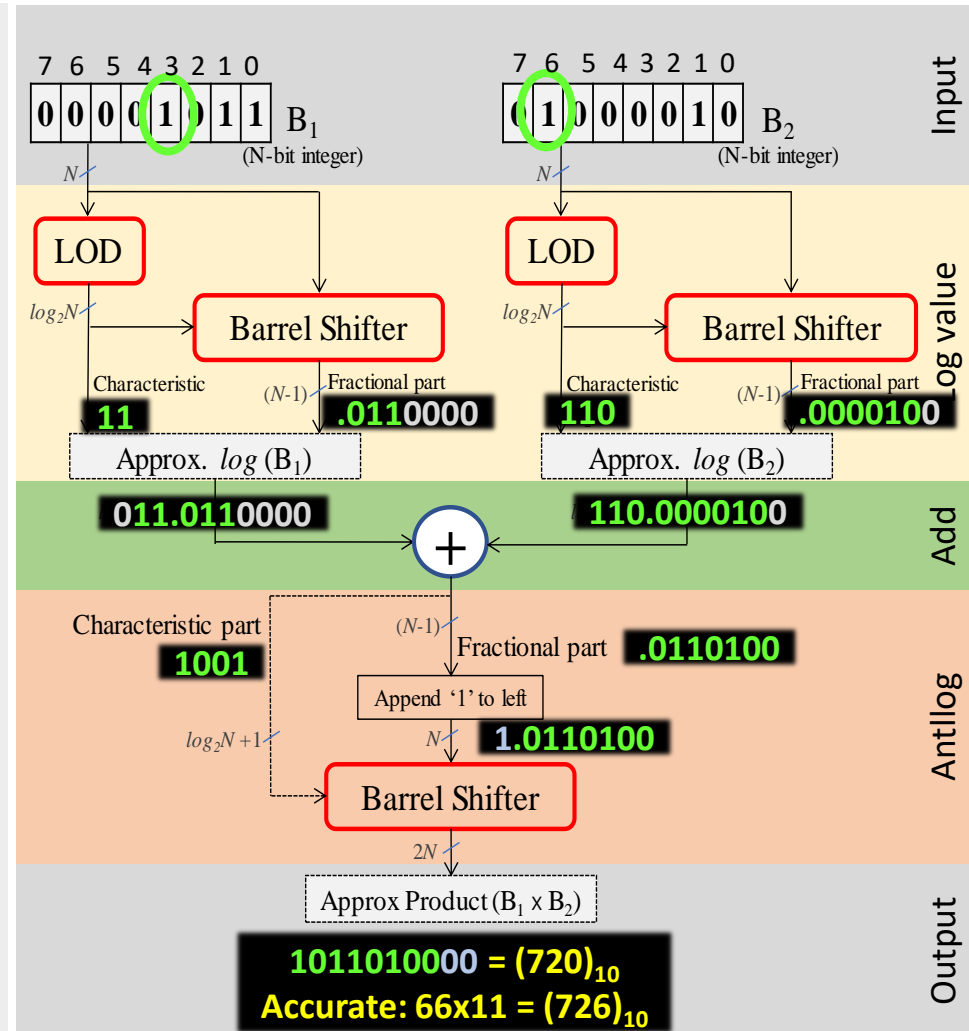$x_1$  and  $x_2$ : fractional part of the log values



# Problem in MA: High and Biased Error

$B_1 \times B_2$

 

$$Error = \begin{cases} 2^{k_1+k_2}(x_1x_2), & x_1 + x_2 < 1 \\ 2^{k_1+k_2}(1 + x_1x_2 - x_1 - x_2), & x_1 + x_2 \geq 1 \end{cases}$$


- Error always has the same sign

Can we do error-correction with minimal overhead?



- Observations

- Error profile is replicated in every power-of-two (pair of  $k_1$  and  $k_2$ )
- Error profile is scaled by  $2^{k_1+k_2}$

Top View

 

Side View

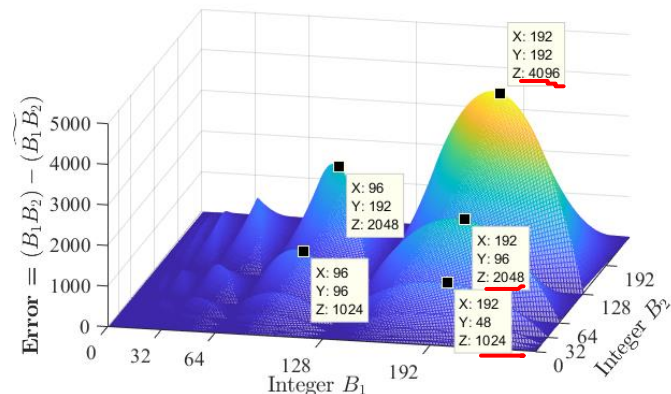 




# Proposed Error Correction: Idea

- Compute mean of error within each interval ( $k_1$  and  $k_2$ )

$$average_{error} = \frac{1}{(1-0)} \frac{1}{(1-0)} \int_0^1 \int_0^1 Error \cdot dx_2 \cdot dx_1 = (0.08333) \times 2^{k_1+k_2}$$

- Add to the approximate product
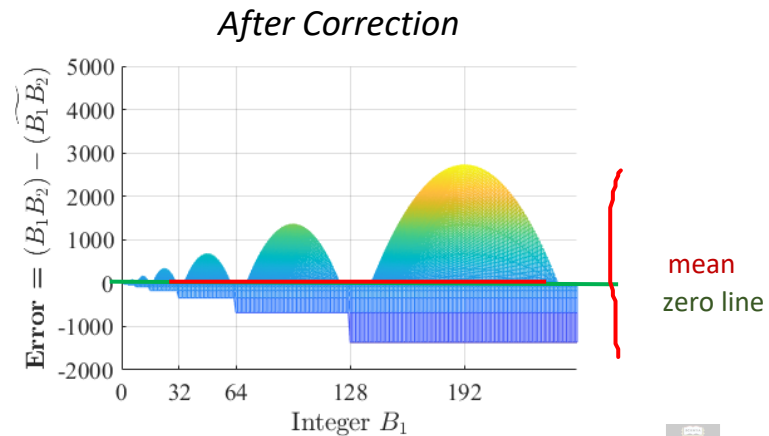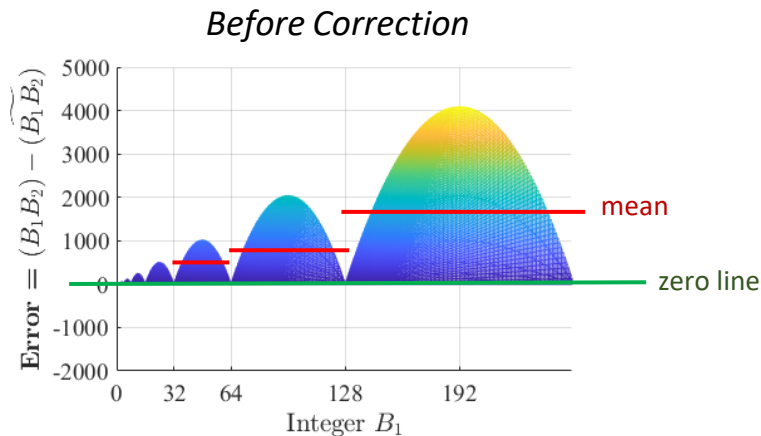 
$$apx\_product = \begin{cases} 2^{k_1+k_2}(1+x_1+x_2), & x_1+x_2 < 1 \\ 2^{k_1+k_2+1}(x_1+x_2), & x_1+x_2 \geq 1 \end{cases} + (0.08333) \times 2^{k_1+k_2}$$






- Independent of integer size  $N$



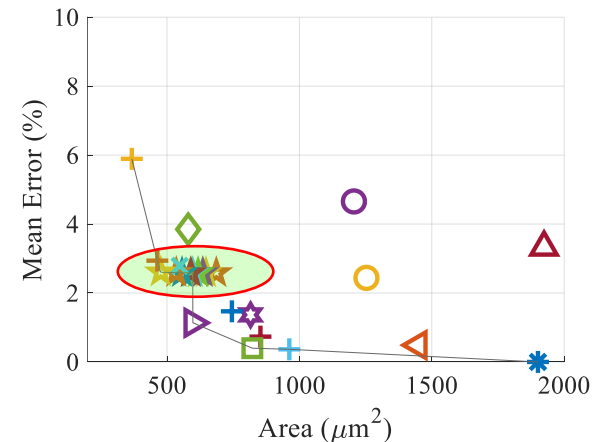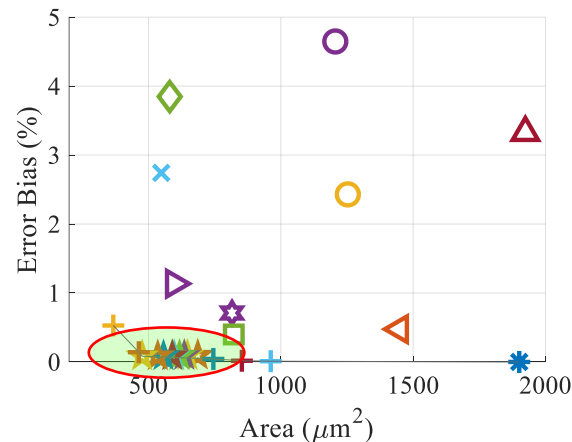
 
# Results – 16-bit Multipliers

- Comparison with state-of-the-art approximate integer multipliers
- Grey line outlines optimal points
- MBM-t gives Pareto optimal points in all!!


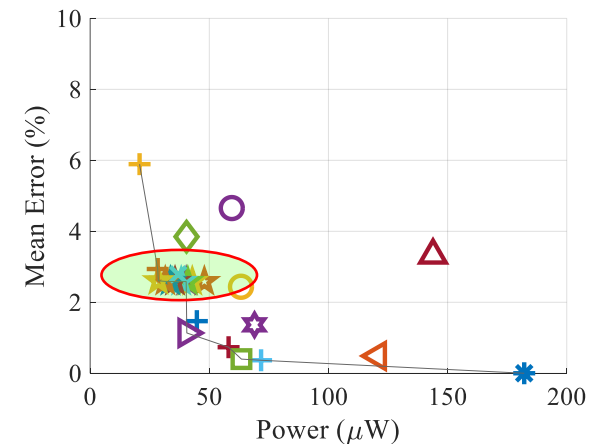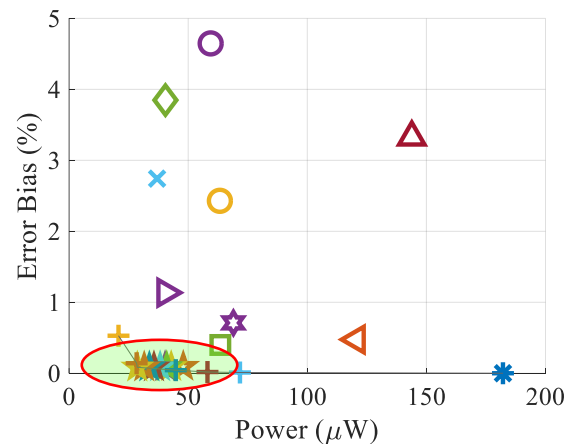
## Experiment Details:

- RTL synthesis using TSMC 45nm at 1GHz
- Error analysis using Monte Carlo simulations
- Error metrics – compared with accurate integer multiplier
  - 1) Error Bias  $\rightarrow$  Mean of Relative Errors
  - 2) Mean Error  $\rightarrow$  Mean of Absolute Relative Errors



# Approximate Multiplier: REALM

---



Quick Overview and Results


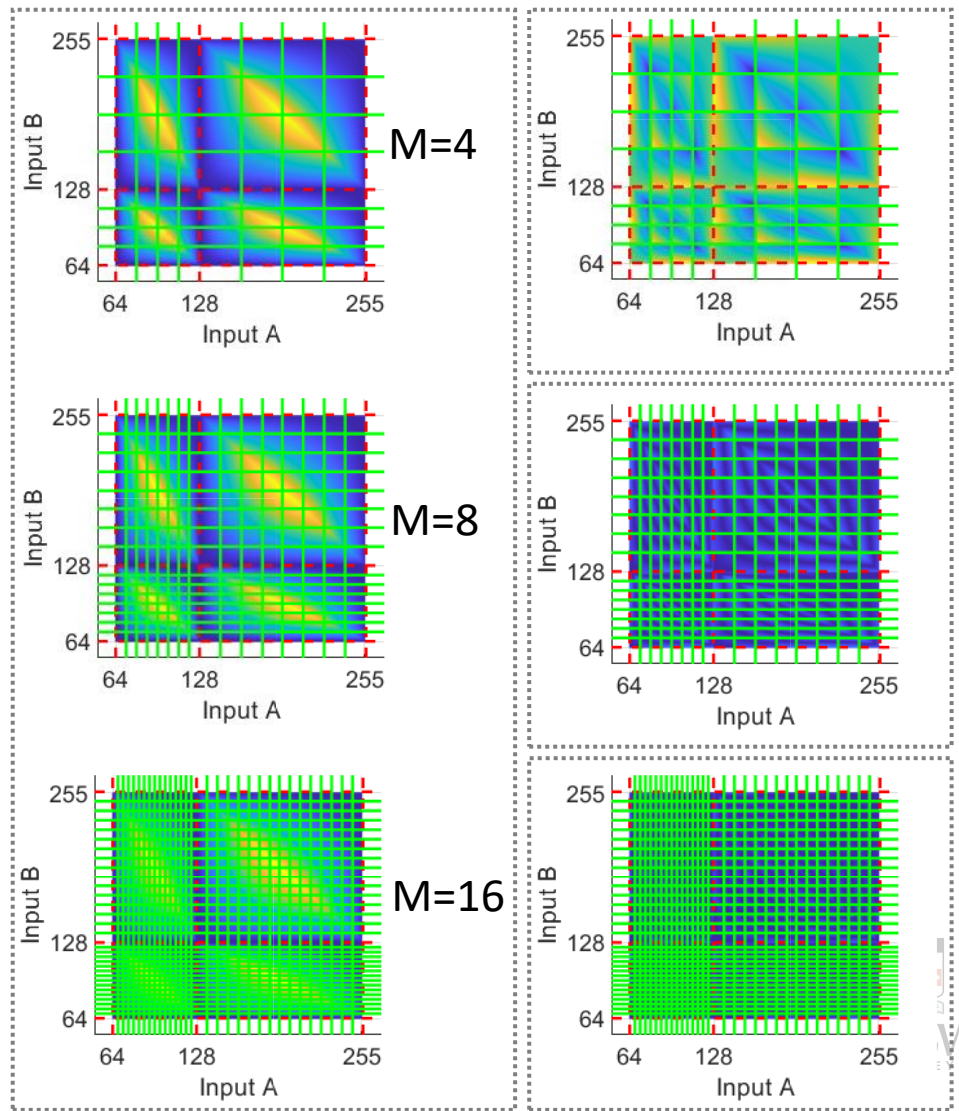 
# REALM Overview

Partition each power-of-two-interval  
into  $M \times M$  segments

Apply error-correction  
on each segment separately




- Number of partitions  $M$  affects the error as well as the hardware cost
- $M$  is an error-configuration knob

# REALM – Hardware design



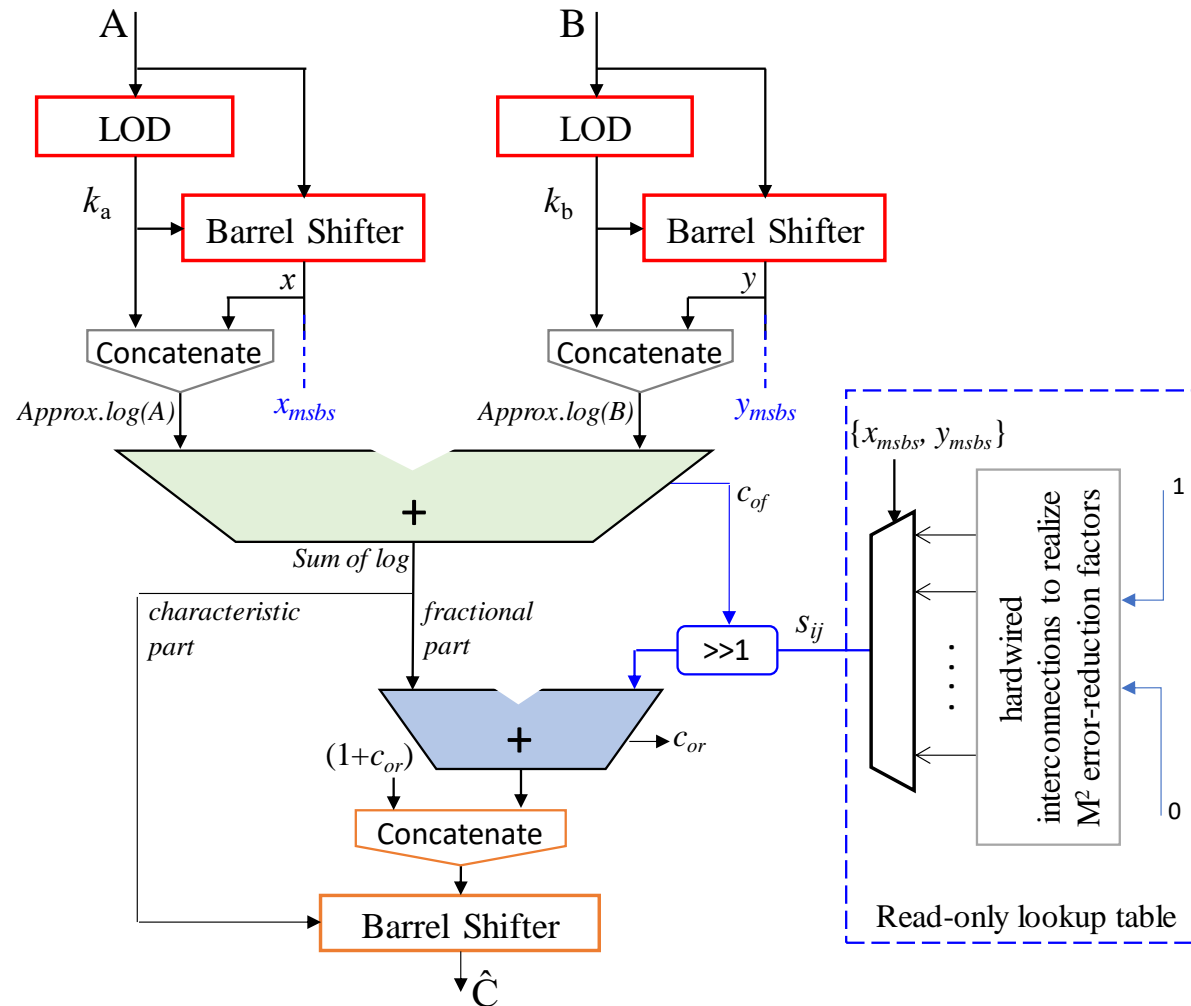
## Proposed REALM

$$\hat{C} = \begin{cases} 2^{k_a+k_b}(1+x+y+s_{ij}), & x+y < 1 \\ 2^{k_a+k_b+1}(x+y+s_{ij}/2), & x+y \geq 1 \end{cases}$$


 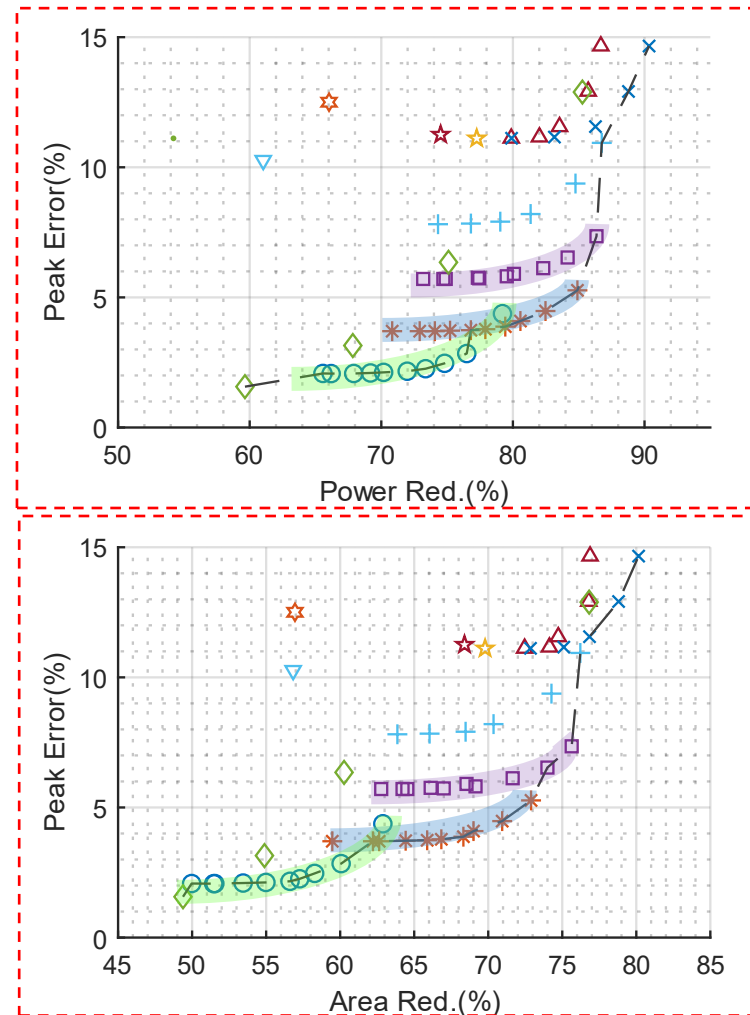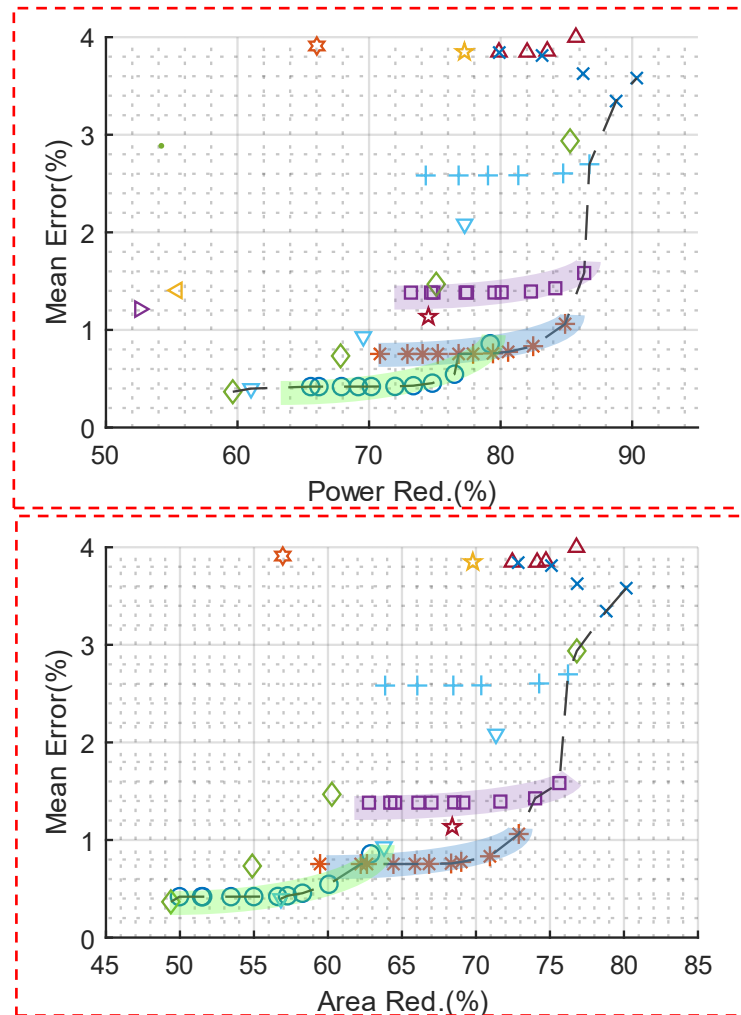
# REALM Results

**REALM** gives Pareto-optimal design points



# References

---

- **Hassaan Saadat**, Haseeb Bokhari, Sri Parameswaran, “Minimally Biased Multipliers for Approximate Integer and Floating-Point Multiplication,” IEEE Transactions on Computer-Aided Design of Integrated Circuits and Systems, 2018. DOI: <https://doi.org/10.1109/TCAD.2018.2857262>
- **Hassaan Saadat**, Haris Javaid, Aleksandar Ignjatovic, Sri Parameswaran, “REALM: Reduced-Error Approximate Log-based Integer Multiplier,” 2020 Design, Automation and Test in Europe Conference and Exhibition (DATE), 2020. DOI: <https://doi.org/10.23919/DATE48585.2020.9116315>

# Questions

---

- Can approximate multipliers be used in LWE cryptography?
- Can you come up with an approximation scheme better suited for this?